

## EXPRRIMENT-5

### Measurement of Self Inductance by Maxwell Bridge


#### AIM

To determine the self-inductance of an unknown coil.

#### Theory

---

This bridge circuit measures an inductance by comparison with variable standard self inductance. The connections for balance condition is shown in Fig. 1.

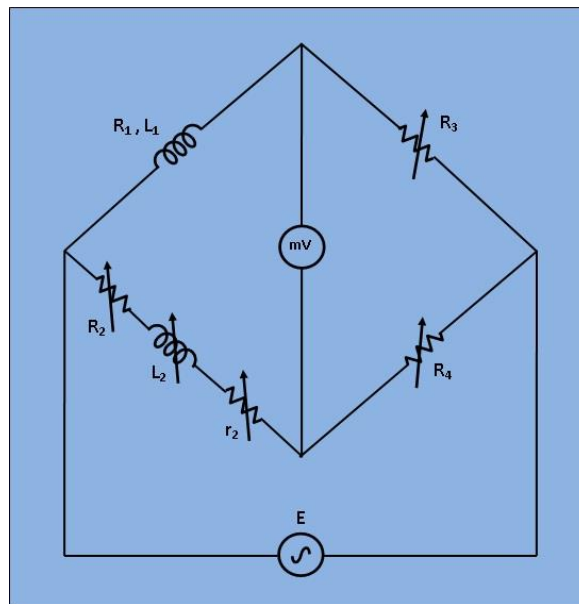

***Fig 1: Circuit Diagram for Measurement of Self Inductance by Maxwell Bridge***

Let,  $L_1$  = Unknown self Inductance of resistance  $R_1$ ,

$L_2$  = variable inductance of fixed resistance  $r_2$ ,

$R_2$  = variable resistance connected in series with inductor  $L_2$ ,

$R_3, R_4$  = known non inductive resistances,

At balance condition,

$$(R_1 + j\omega L_1) * R_4 = (R_2 + r_2 + j\omega L_2) * R_3 \dots (1)$$


Equating both the real and imaginary parts in eq.(1) and separating them,

$$L_1 = \left(\frac{R_3}{R_4}\right)L_2 \dots (2)$$

$$R_1 = \left(\frac{R_3}{R_4}\right) * (R_2 + r_2) \dots (3)$$

Resistors  $R_3$  and  $R_4$  are normally a selection of values from 10, 100, 1000 and 10,000 $\Omega$ .  $r_2$  is a decade resistance box.

## Procedure

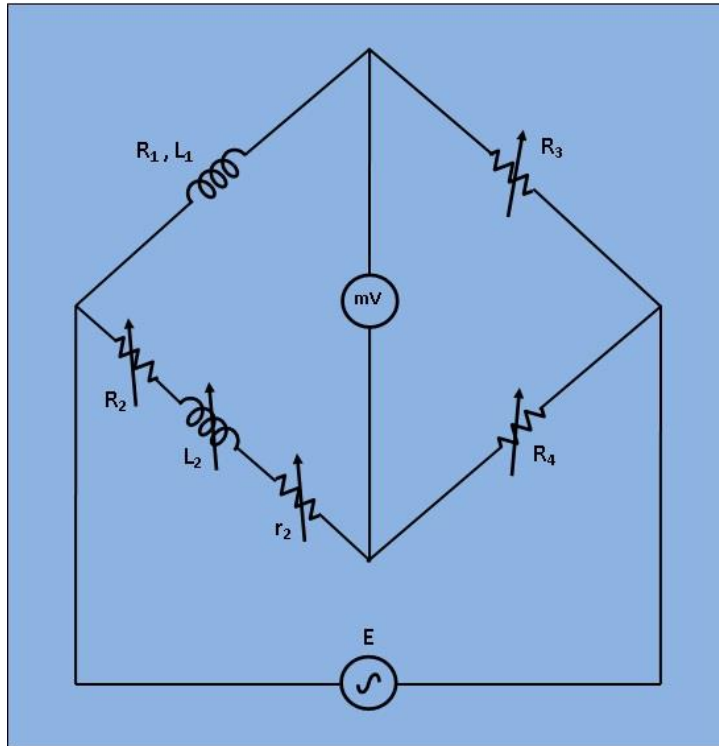

**Fig 1: Circuit Diagram for Measurement of Self Inductance by Maxwell Bridge**

1. Apply Supply voltage from the signal generator with arbitrary frequency. ( $V = 3V$ ). Also set the unknown Inductance value from 'Set Inductor Value' tab.
2. Then switch on the supply to get millivoltmeter deflection.
3. Choose the values of  $L_2$ ,  $r_2$ ,  $R_2$ ,  $R_3$  and  $R_4$  from the inductance and resistance box. Vary the values to some particular values to achieve "NULL".
4. Observe the millivoltmeter pointer to achieve "NULL".
5. If "NULL" is achieved, switch to 'Measure Inductor Value' tab and click on 'Simulate'. Observe the calculated values of unknown inductance ( $L_1$ ) and it's


internal resistance ( $R_1$ ) of the inductor.

6. Also observe the Dissipation factor of the unknown inductor which is defined as


$$\frac{\omega L}{R} \text{ Where, } \omega = 2\pi f$$

## SIMULATION


### AIR CORE

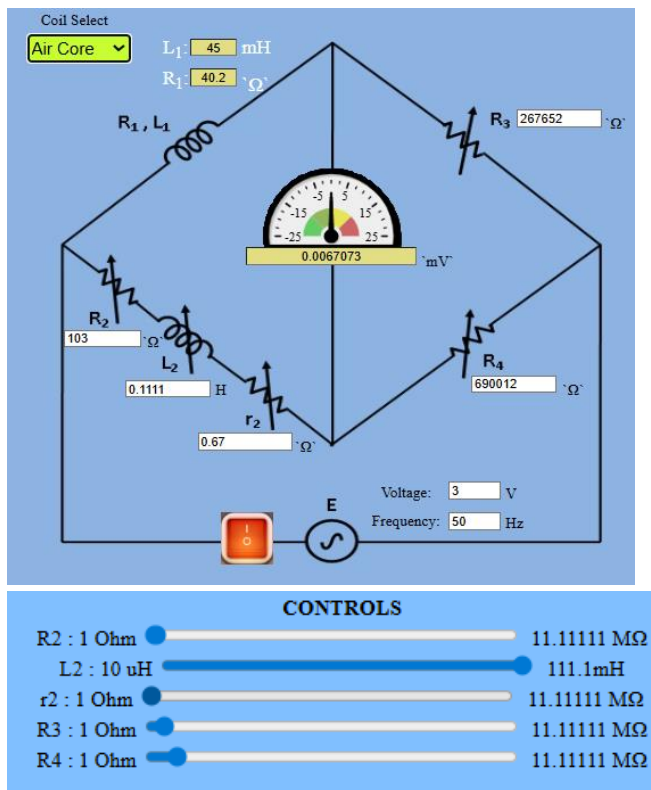

### Measure Inductor Value

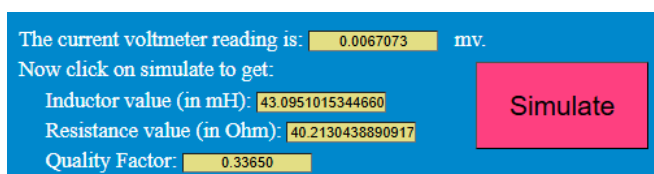

## IRON CORE

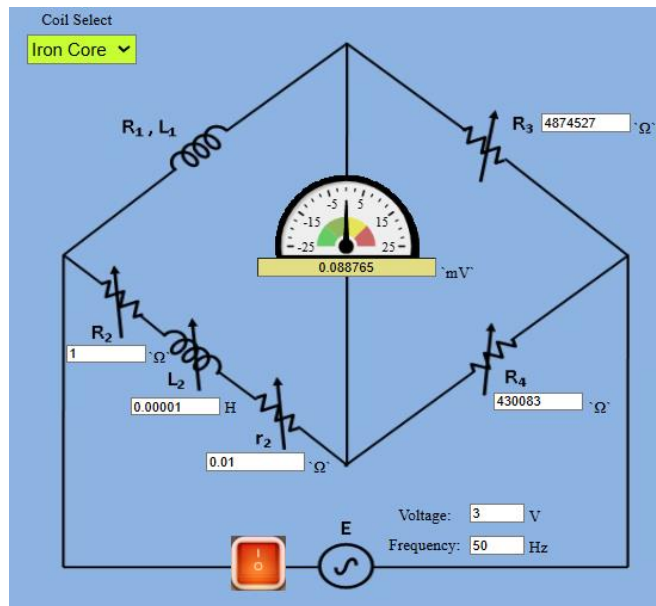

CONTROLS		
R2 : 1 Ohm	<input type="range"/>	11.11111 M $\Omega$
L2 : 10 uH	<input type="range"/>	111.1mH
r2 : 1 Ohm	<input type="range"/>	11.11111 M $\Omega$
R3 : 1 Ohm	<input type="range"/>	11.11111 M $\Omega$
R4 : 1 Ohm	<input type="range"/>	11.11111 M $\Omega$

## Measure Inductor Value

The current voltmeter reading is: 0.088765 mv.

Now click on simulate to get:

Inductor value (in mH):	0.11333921591878
Resistance value (in Ohm):	11.4472608077975
Quality Factor:	0.0031089

## RESULT

Thus the unknown inductance is found using maxwell bridge

